

Quantization Noise in ADCs

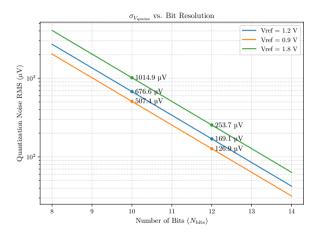



$$\sigma_{V_{
m qnoise}} = rac{2V_{
m ref}}{2^N\sqrt{12}}$$

Sampling Noise in SAR ADCs

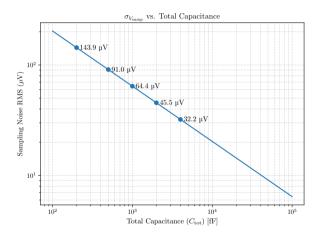

ENOB vs C_{tot}: Sampling Noise

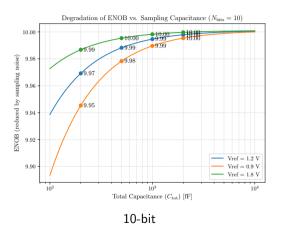

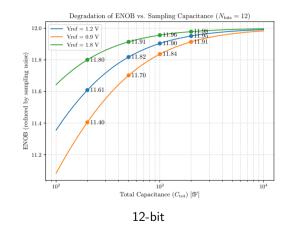


Unit Fringe Capacitor


1 layer: $0.31 \text{ fF}/\mu\text{m}^2$ 2 layers: $0.62 \text{ fF}/\mu\text{m}^2$ 3 layers: $0.93 \text{ fF}/\mu\text{m}^2$ Matching coefficient:
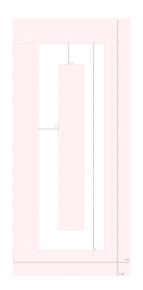
$$\sigma(\Delta C/C) = 0.85\% \times \sqrt{C \text{ [fF]}}$$






Expected Mismatch and DNL Noise

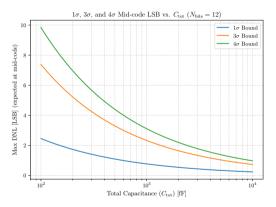


Expected Mismatch (12-bit)

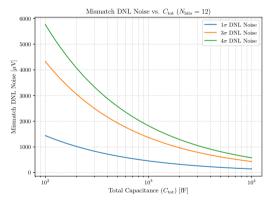

DNL Noise from Mismatch (12-bit)

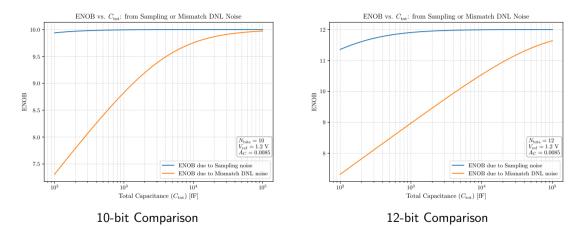ENOB vs Ctot: Sampling Noise or Mismatch DNL Noise



Note: Assuming a worst case 3σ variation, corresponding to roughly 1 in 300 ADCs

CDAC Array Overview

