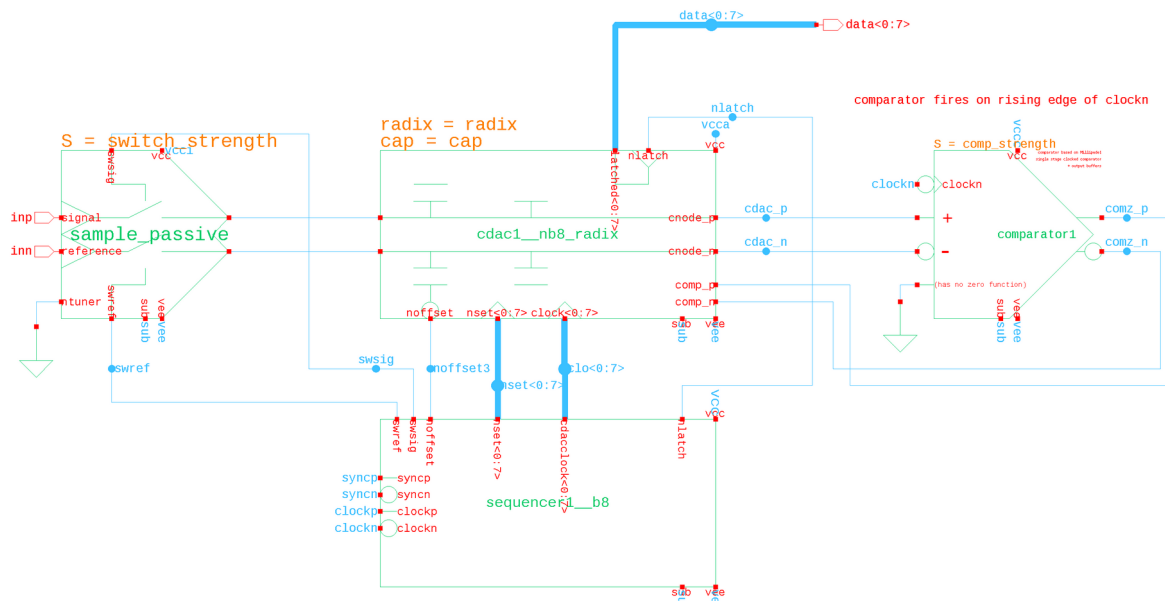


# What's the goal?

Design	EDET DCD	CoRDIA	pre-Helena	Helena
ADC resolution	8-bit	10-bit	8-bit	10-bit
Conversion rate	10 MHz	2.5MHz	5 MHz	10 MHz
Area of one ADC	100x200 $\mu\text{m}^2$	80x330 $\mu\text{m}^2$	60x800 $\mu\text{m}^2$	20x100 $\mu\text{m}^2$
Power of one ADC	1800 $\mu\text{W}$	30 $\mu\text{W}$	700 $\mu\text{W}$	100 $\mu\text{W}$
FOM_csa (conv/sec/area)	500 Hz/ $\mu\text{m}^2$	95 Hz/ $\mu\text{m}^2$	105 Hz/ $\mu\text{m}^2$	5000 Hz/ $\mu\text{m}^2$
FOM_epc (energy/conv)	180 pJ	12 pJ	155 pJ	10 pJ
FOM_ppa (power/area)	9.0 W/cm <sup>2</sup>	0.11 W/cm <sup>2</sup>	1.45 W/cm <sup>2</sup>	5.0 W/cm <sup>2</sup>
ADC qty Mpix @ 100 KHz	10000	40000	20000	10000
ADCs total pixel rate	100 Gpx/s	100 Gpx/s	100 Gpx/s	100 Gpx/s
ADCs total data rate	800 Gb/s	1 Tb/s	800 Gb/s	1 Tb/s
ADCs total area	2.0 cm <sup>2</sup>	10.5 cm <sup>2</sup>	9.6 cm <sup>2</sup>	0.2 cm <sup>2</sup>
ADCs total power	35.0 W	1.2 W	14 W	1.0 W




## What should we try tuning?

- ✓ capacitor array radix ratio & repetitions
- ✓ capacitor array unit & repetitions total values
- ✓ capacitor array switching scheme? (monotonic is simple)
- ✓ comparator architecture and strength
- ✓ total ADC nominal resolution
- ✓ total comparisons & time per comparison

**SPICE @ 100 samples per bin:**

8-bit ADC: ~15 hours  
10-bit ADC: ~2.5 days

## Schematic setup: Principles

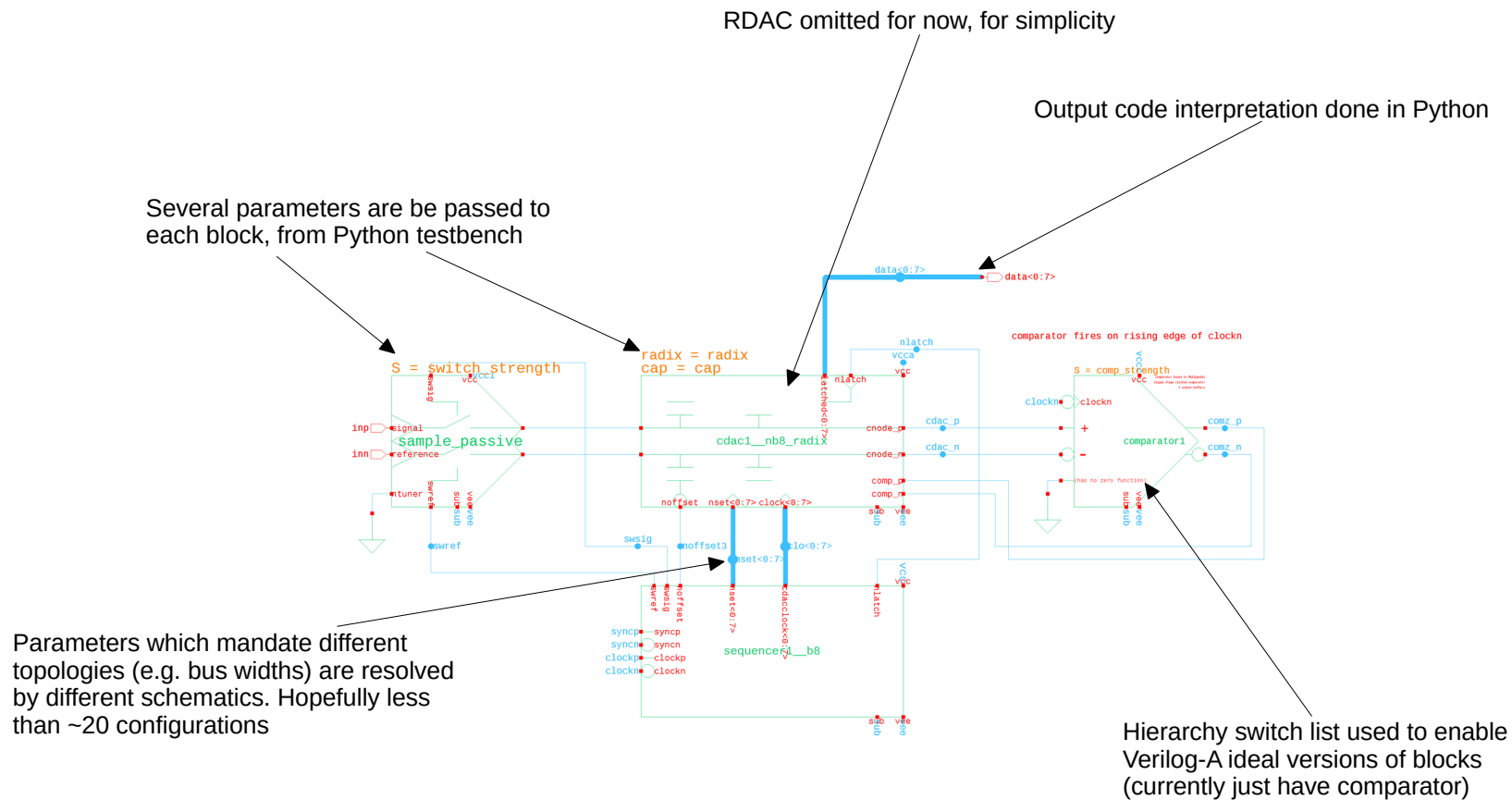


# Model parameters

```
params = {
  "ADC": {
    "bit_size": 8,                # nominal resolution of the ADC (switching between netlists)
    "sampling_frequency": 10.0e6, # sampling rate in Hz, used to driver clock sources
    "jitter": 0.0e-12,           # aperture jitter in seconds (TBD)
    "device_noise": False,       # enables basic gaussian noise in behavioral, and tran noise in SPICE
  },
  "TESTBENCH": {
    "positive_input_voltages": [0.2, 1.2, 20e-6], # start, end (incl.), and step voltage
    "negative_input_voltages": [1.2, 0.2, 20e-6],
    "use_calibration": False, # account for cap error when calculating Dout (re-analog)
    "pdk_file": "\\~\\helena\\tech\\tsmc65\\default_testbench_header_55ulp_linux.lib\\\" tt",
    "spicedir": None, # Use this to write netlist from template
    "rawdir": None, # Use this to set SPICE output dir, and to read for parsing
  },
  "SWITCH": {
    "offset_voltage": 0.0e-3, # offset voltage in Volts
    "common_mode_dependent_offset_gain": 0.0, # common mode voltage gain
    "threshold_voltage_noise": True,
    "type": "passive", # supports active, passive, or ideal
    "strength": 4,
  },
  "COMP": {
    "offset_voltage": 0.0e-3, # offset voltage in Volts
    "common_mode_dependent_offset_gain": 0.0, # common mode voltage gain
    "threshold_voltage_noise": True,
    "strength": 4, # used to size some active devices (SPICE only)
  },
  "CDAC": {
    "positive_reference_voltage": 1.2, # reference voltage in Volts
    "negative_reference_voltage": 0.0, # reference voltage in Volts
    "reference_voltage_noise": 0.0e-3, # reference voltage noise in Volts (CDAC)
    "switching_strat": "monotonic", # {monotonic, bss} used to determined initial starting voltages
    "unit_capacitance": 1e-15, # unit capacitance
    "target_capacitance": None, # Used for alternative
    "array_size": 8, # number of capacitor stages
    "array_N_M_expansion": False, # Sizing strategy where
    "multiple_conversions": None, # List bit positions in C array, with number of repetitions at each
    "use_rdac": False, # Set bit position which should
    "use_offset_cap": False, # set to 0 farads, if disabled
    "use_split_cap": True, # set to 0 farads, if disabled
    "parasitic_capacitance": 5.00e-14, # estimate of capacitance at output (added to SPICE and ideal)
    "settling_time": 0.0e-9, # individual settling errors per capacitor?
  },
}
```


! Work in progress !
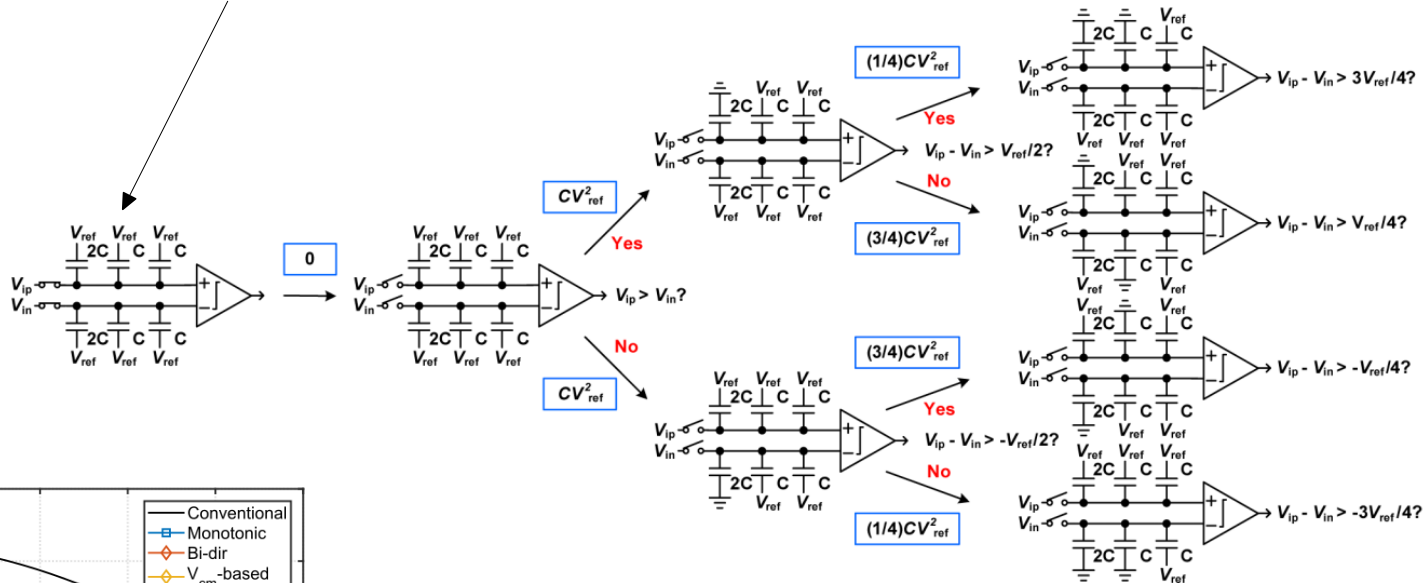
# CDAC model parameters: Switching scheme

Initial values of bottom-plate voltages differentiate 'Monotonic' vs 'BSS' switching



[C.C. Liu JSSC 2010]

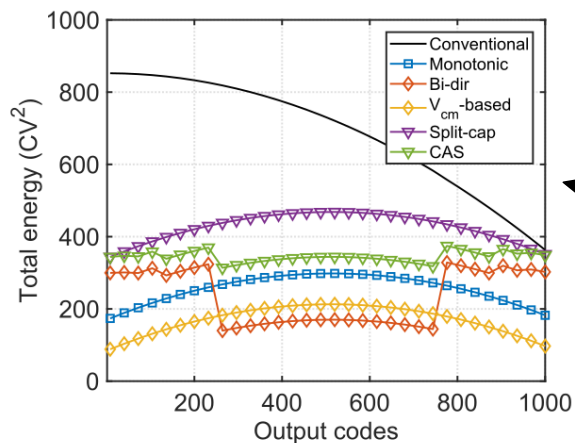

Other schemes require different topology but we already have good energy savings

[X. Tang IEEE TCAS 2022]

# CDAC model parameters: Capacitor calculation

$N_{CDAC}$  number of capacitor stages (on both N and P plate)

$\beta$  radix: 2.0, 1.85, 1.8, etc

Approach #1:  
thinking in terms of  
LSB capacitor size

$C_{unit}$  typically ~1 fF

where  $i = 0, 1, 2, \dots, (N_{CDAC} - 1)$

$$w_i = \beta^i$$

weights

$$C_i = C_{unit} \cdot w_i$$

capacitor values

Approach #2: If we care  
about total capacitance

$C_{total}$  typically ~ 100 fF

where  $i = 0, 1, 2, \dots, (N_{CDAC} - 1)$

$$C_i = \frac{C_{total}}{2 \cdot \beta^{(N_{CDAC}-1-i)}} \quad \text{capacitor values}$$


$$w_i = \frac{C_i}{C_0} \quad \text{weights}$$

```
>>> w_radix1p8 = [2.0**i for i in range(8)]  
[1.0, 2.0, 4.0, 8.0, 16.0, 32.0, 64.0, 128.0]
```

```
>>> w_radix2 = [1.8**i for i in range(8)]  
[1.0, 1.8, 3.24, 5.83, 10.5, 18.9, 34.01, 61.22]
```

Approach #3: If we care  
about allowable input signal  
swing, account for split  
offset and parasitic caps
 
# CDAC model parameters: Input voltage swings



✗ The differential input range is limited by the CDAC and additional + parasitic caps

In this 9-bit 1.2V ref case:  $\Delta V_{in} \approx \frac{C_{dac}}{C_{total}} \cdot V_{ref} = \frac{136}{61 + 136} \cdot 1.2 = 0.826$


✗ Also note, non-ideal comparator has common-mode input limitation

# CDAC model parameters: Settling error


Monotonic switching ameliorates RC delay, but it will still manifest as voltage error when:

- ✗ Clock periods are short
- ✗ Differential input voltage is large
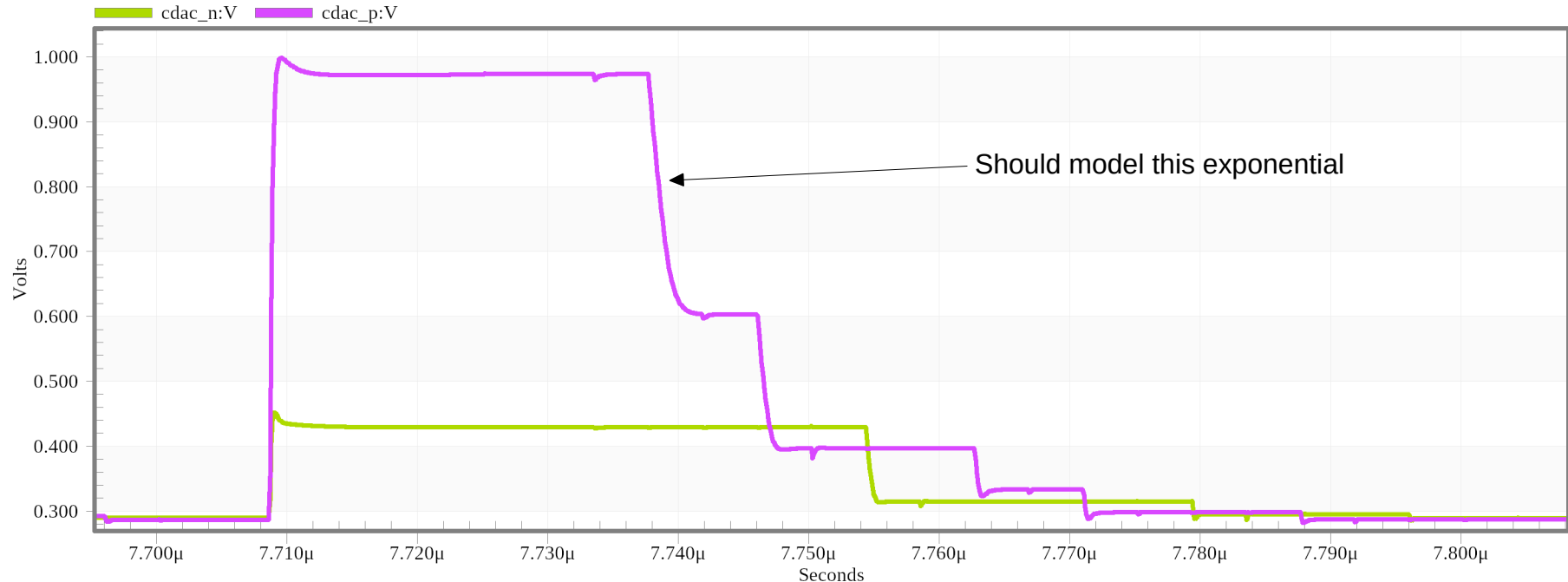
$$\text{settling\_time\_error} = e^{-\frac{1}{\tau_s \cdot f_s \cdot (N+1)}}$$


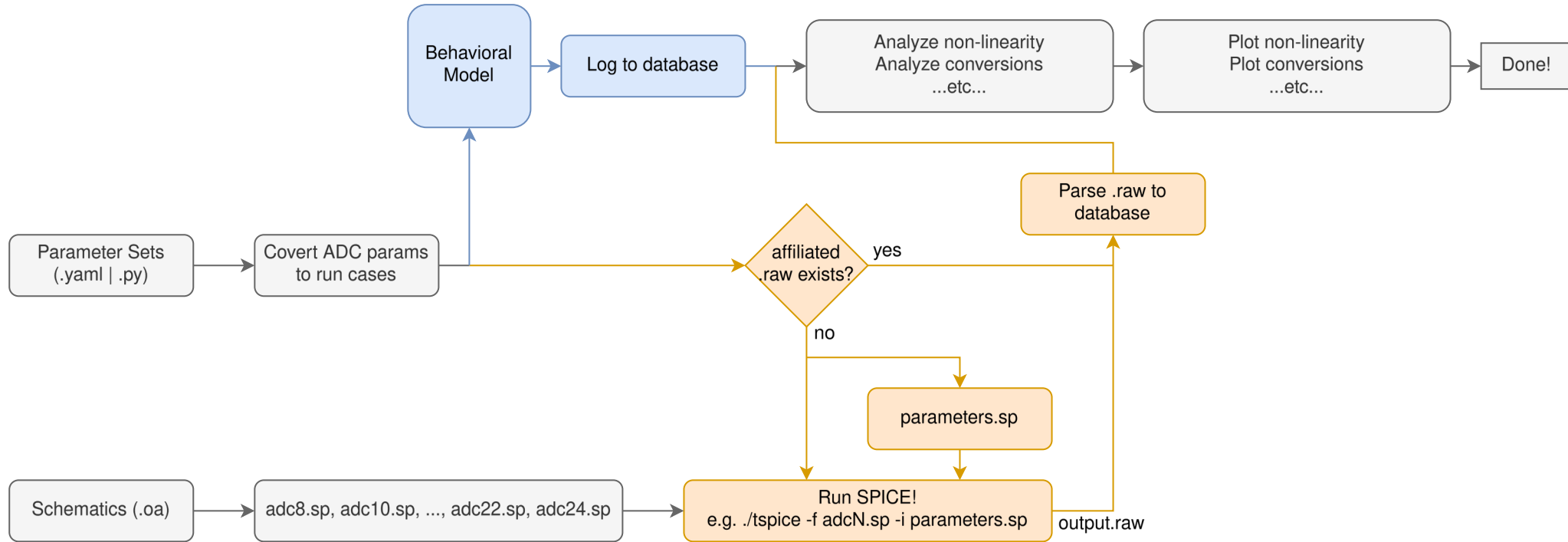
# Workflow: SPICE & behavioral models use same params



Tried with Spectre/AFS but  
.scs format is very different



# Testbench parameters: Syncing input voltages and clocks


```
-----Behavioral dataframe-----  
                Vin  
0      -0.59999333  
1      -0.59996000  
2      -0.59992667  
3      -0.59989333  
4      -0.59986000  
...      ...  
35995   0.59986000  
35996   0.59989333  
35997   0.59992667  
35998   0.59996000  
35999   0.59999333
```

```
-----SPICE dataframe-----  
                Vin  
0      -0.59994  
1      -0.59991  
2      -0.59988  
3      -0.59985  
4      -0.59982  
...      ...  
39991   0.59982  
39992   0.59985  
39993   0.59988  
39994   0.59991  
39995   0.59994
```



Because we are trying to directly compare  
SPICE vs behavioral data, it's best if the  
timing and voltage references are synced

We can correct this with  
Verilog-A models which are  
easier to handle than SPICE  
primitives

```
`include "discipline.h"  
`include "constants.h"  
  
module vstepper(vstart, vstep, vend, clk, vout);  
    input vstart, vstep, vend, clk;  
    output vout;  
    electrical vstart, vstep, vend, clk, vout;  
  
    // Internal variable to store the current voltage  
    real current_voltage;  
    real next_update_time;  
  
    // Initial conditions  
    initial begin  
        current_voltage = vstart; // Start voltage is vstart  
        next_update_time = $abstime; // Initialize the update time  
    end  
  
    // Voltage update logic  
    analog begin  
        // Only update the voltage when the clock signal is active (high)  
        if (V(clk) > 0) begin  
            // If the current voltage is less than vend, increment  
            if (current_voltage < V(vend)) begin  
                current_voltage = current_voltage + V(vstep);  
                if (current_voltage > V(vend)) begin  
                    current_voltage = V(vend); // Ensure voltage doesn't exceed vend  
                end  
            end  
        end  
    end  
  
    // Output the current voltage  
    V(vout) <+ current_voltage;  
  
end  
  
endmodule // vstepper
```

 

# Does the behavioral model work?

  

✓ yep,  
for (most)  
Vin values

# Testbench: Output value calculation (i.e. 're-analog')

$$R = \sum_{i=0}^{N_{CDAC}-1} b_i \cdot w_i$$

where  $i = 0, 1, 2, \dots, (N_{CDAC} - 1)$

$$w_i = \beta^i$$

cycles = 1, 2, 3, 4, 5, 6, 7, 8

weights =  $w_i = w_7, w_6, w_5, w_4, w_3, w_2, w_1, w_0$

SA register =  $r_i = r_7, r_6, r_5, r_4, r_3, r_2, r_1, r_0$

data out =  $b_i = b_7, b_6, b_5, b_4, b_3, b_2, b_1, b_0$

8-capacitor  
CDAC/ADC

Equivalent expression  
(except 0 → 1 range)

radix = 2  
dac16\_radix  
dac16\_radix\_2

0, 0, 0, 0, 0, 0, 0, 0, data<0:7> in<0:15> out reanalog\_b8

.subckt dac16\_radix in<0> in<1> in<2> in<3> in<4> in<5>  
+ in<6> in<7> in<8> in<9> in<10> in<11> in<12> in<13>  
+ in<14> in<15> out radix=1.8 (default value)

eout out gnd vol='  
V(in<15>)/pow(radix, 0)+  
V(in<14>)/pow(radix, 1)+  
V(in<13>)/pow(radix, 2)+  
V(in<12>)/pow(radix, 3)+  
V(in<11>)/pow(radix, 4)+  
V(in<10>)/pow(radix, 5)+  
V(in<9>)/pow(radix, 6)+  
V(in<8>)/pow(radix, 7)+  
V(in<7>)/pow(radix, 8)+  
V(in<6>)/pow(radix, 9)+  
V(in<5>)/pow(radix, 10)+  
V(in<4>)/pow(radix, 11)+  
V(in<3>)/pow(radix, 12)+  
V(in<2>)/pow(radix, 13)+  
V(in<1>)/pow(radix, 14)+  
V(in<0>)/pow(radix, 15)'  
.ends

```
>>> w_radix2 = [2.0**i for i in range(8)]
[1.0, 2.0, 4.0, 8.0, 16.0, 32.0, 64.0, 128.0]
```

```
>>> sum(w_radix2)
255.0
```

```
>>> w_radix1p8 = [1.8**i for i in range(8)]
[1.0, 1.8, 3.24, 5.83, 10.5, 18.9, 34.01, 61.22]
```

```
>>> sum(w_radix1p8)
136.4995072
```


# Testbench: Output value calculation (i.e. 're-analog')

$$R = \sum_{i=0}^{N_{CDAC}-1} b_i \cdot w_i$$


$$w_i = \beta^i$$

where  $i = 0, 1, 2, \dots, (N_{CDAC} - 1)$


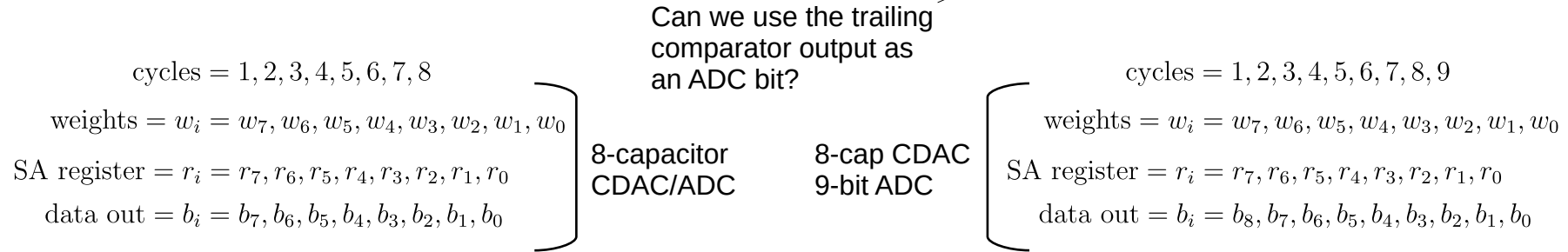
$$R = \sum_{i=1}^{N_{CDAC}} (2 \cdot b_i - 1) \cdot w_{i-1} + b_0 - 1$$


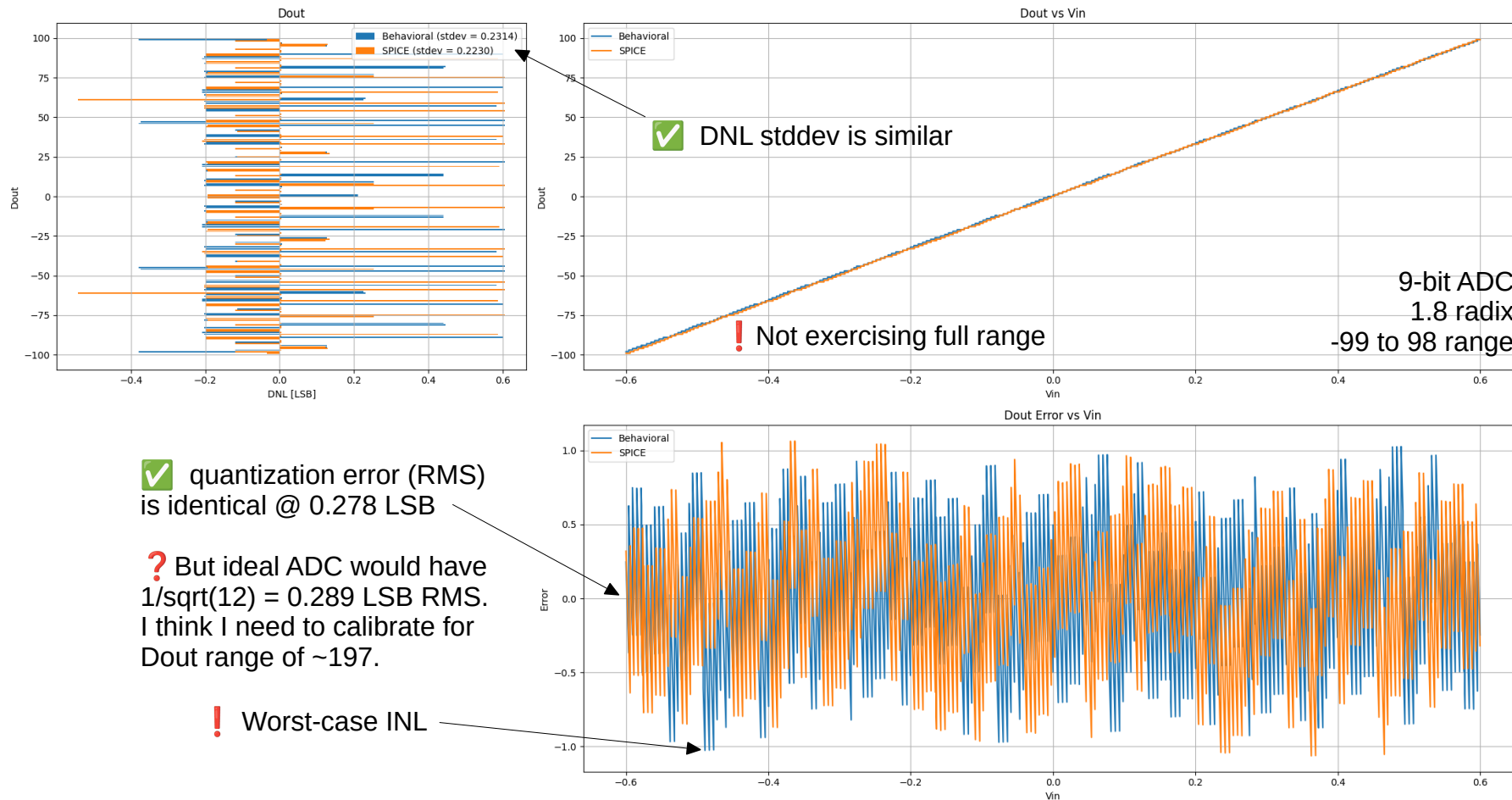
# Behavioral vs SPICE: Linearity comparison


 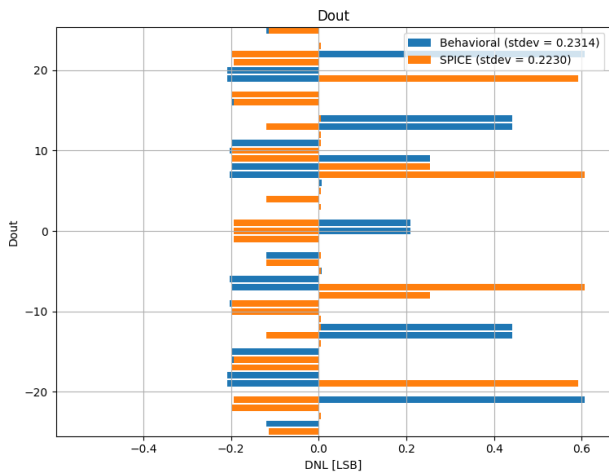
# Behavioral vs SPICE: Linearity comparison




✗ 1 LSB errors exist

Is rounding applied at different stages?



Perhaps parasitic capacitance is throwing us off? I calculated ~50 fF for the parasitics plus

```
-----Behavioral dataframe-----
  Vin      Dout      Dout_rounded
0 -0.59999333 -98.2403072 -98.0
1 -0.59996000 -98.2403072 -98.0
2 -0.59992667 -98.2403072 -98.0
3 -0.59989333 -98.2403072 -98.0
4 -0.59986000 -98.2403072 -98.0
...
35995 0.59986000 99.2403072 99.0
35996 0.59989333 99.2403072 99.0
35997 0.59992667 99.2403072 99.0
35998 0.59996000 99.2403072 99.0
35999 0.59999333 99.2403072 99.0
```
 
```
-----SPICE dataframe-----
  Vin      Dout      Dout_rounded
0 -0.59994 -98.7403072 -99.0
1 -0.59991 -98.7403072 -99.0
2 -0.59988 -98.7403072 -99.0
3 -0.59985 -98.7403072 -99.0
4 -0.59982 -98.7403072 -99.0
...
39991 0.59982 98.7403072 99.0
39992 0.59985 98.7403072 99.0
39993 0.59988 98.7403072 99.0
39994 0.59991 98.7403072 99.0
39995 0.59994 98.7403072 99.0
```



  
# Behavioral vs SPICE: Linearity comparison







comp	data<0>	data<1>	data<2>	data<3>	data<4>	data<5>	data<6>	data<7>
0	1	1	0	0	1	0	1	1
1	1	1	0	0	1	1	1	1
0	0	0	1	0	1	0	1	1
1	0	0	1	0	1	0	1	1

Vin	Dout
0.48723	79.564147
0.48990	80.564147
0.48993	80.444147
0.49257	81.444147

 ? Some codes are non-monotonic, in both SPICE and behavioral models?



 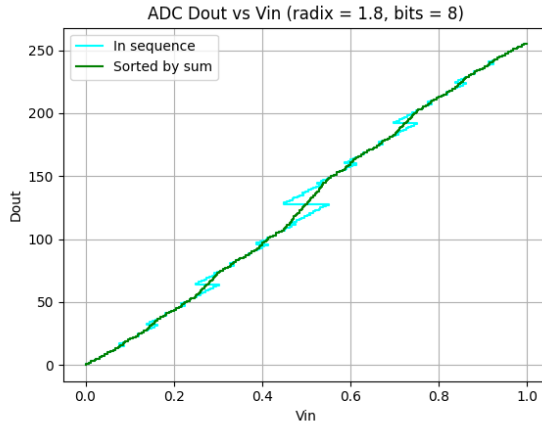  
# How are non-binary redundant codes distributed?






# What about double conversions?


Conventional binary

 

Non-binary  
(integer rounded weights)

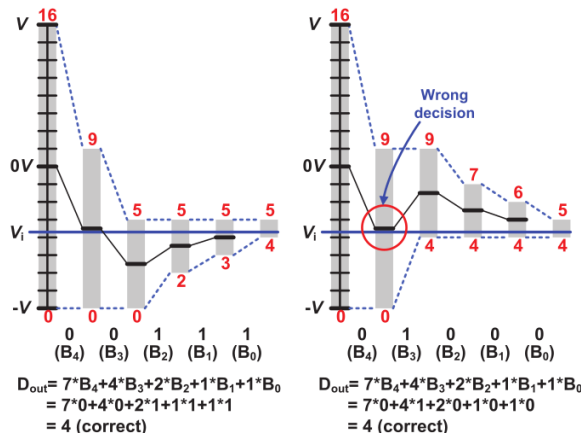

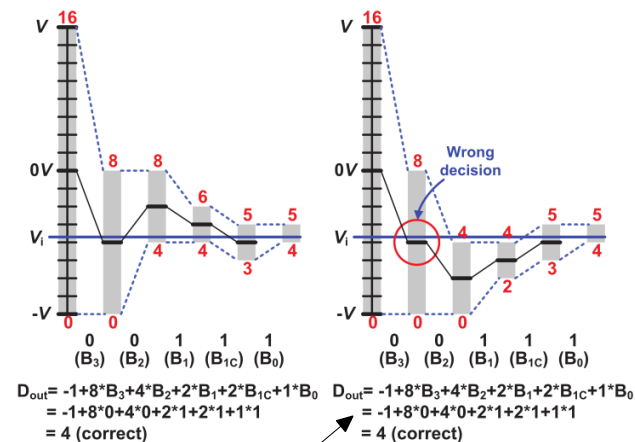“Binary-scaled  
compensation/recombination”



The repeated conversion steps need an offset of half their weight to account for the ‘bias’ they introduce

```

params = {
  "ADC": {
    "bit_size": 8,                # nominal resolution of the ADC (switching between netlists)
    "sampling_frequency": 10.0e6, # sampling rate in Hz, used to driver clock sources
    "jitter": 0.0e-12,           # aperture jitter in seconds (TBD)
    "device_noise": False,       # enables basic gaussian noise in behavioral, and tran noise in SPICE
  },
  "TESTBENCH": {
    "positive_input_voltages": [0.2, 1.2, 20e-6], # start, end (incl.), and step voltage
    "negative_input_voltages": [1.2, 0.2, 20e-6],
    "use_calibration": False, # account for cap error when calculating Dout (re-analog)
    "pdk_file": "\\~\\helena\\tech\\tsmc65\\default_testbench_header_55ulp_linux.lib\\\" tt\",
    "spicedir": None, # Use this to write netlist from template
    "rawdir": None, # Use this to set SPICE output dir, and to read for parsing
  },
  "SWITCH": {
    "offset_voltage": 0.0e-3, # offset voltage in Volts
    "common_mode_dependent_offset_gain": 0.0, # common mode voltage gain
    "threshold_voltage_noise": True,
    "type": "passive", # supports active, passive, or ideal
    "strength": 4,
  },
  "COMP": {
    "offset_voltage": 0.0e-3, # offset voltage in Volts
    "common_mode_dependent_offset_gain": 0.0, # common mode voltage gain
    "threshold_voltage_noise": True,
    "strength": 4, # used to size some active devices (SPICE only)
  },
  "CDAC": {
    "positive_reference_voltage": 1.2, # reference voltage in Volts
    "negative_reference_voltage": 0.0, # reference voltage in Volts
    "reference_voltage_noise": 0.0e-3, # reference voltage noise in Volts (CDAC)
    "switching_strat": "monotonic", # {monotonic, bss} used to determined initial starting voltages
    "unit_capacitance": 1e-15, # unit capacitance
    "target_capacitance": None, # Used for alternative
    "array_size": 8, # number of capacitor stages
    "array_N_M_expansion": False, # Sizing strategy where
    "multiple_conversions": None, # List bit positions in C array, with number of repetitions at each
    "use_rdac": False, # Set bit position which should
    "use_offset_cap": False, # set to 0 farads, if disabled
    "use_split_cap": True, # set to 0 farads, if disabled
    "parasitic_capacitance": 5.00e-14, # estimate of capacitance at output (added to SPICE and ideal)
    "settling_time": 0.0e-9, # individual settling errors per capacitor?
  },
}

```

# Next steps?